

**Q-3** Explain Shift –Left register and Shift –Right register in detail with block diagram.